

## One mark Question with Answer - COA

1. A gate is a logic circuit with one or more input signal but \_\_\_\_\_ output signal.
2. The Exclusive –NOR gate is equivalent to an \_\_\_\_\_ gate followed by an inverter.
3. De-multiplexer is also known as \_\_\_\_\_.
4. A register is a group of \_\_\_\_\_ with each flip flop capable of storing 1 bit of information.
5. A flip-flop can store \_\_\_\_\_ bit off duty.
6. An inverter is also called a \_\_\_\_\_ gate.
7. The NAND function is the complement of the AND function. True or False?
8. AND, OR, and NOT are considered as universal gate. True or False?
9. In Half Adder the outputs X-OR gate is \_\_\_\_\_.
10. Full name of SISO \_\_\_\_\_.
11. A Three input NOR gate logic high output only when \_\_\_\_\_.
12. Full name of VLSI \_\_\_\_\_.
13. One byte= \_\_\_\_\_ bits.
14. The K-MAP is also known as \_\_\_\_\_ diagram.
15. If both input is high then what is output in NAND gate?
16. Which combinational circuit adds two binary bits?
17. A XOR gate has input A and B and output Y. Then the output equation is \_\_\_\_\_.
18. Demorgan's theorem is \_\_\_\_\_.
19. JK flip-flop is Universal flip-flop? (True/False).
20.  $J=1, K=1$  is a J-K flip-flop made to toggle? (True/False).
21. An example of SOP expression is \_\_\_\_\_.
22. On a karnaugh map, grouping the 0s produces a \_\_\_\_\_.
23. After counting 00, 01, \_\_, 11.
24. SR flip-flop is face the indeterminate condition problem? (True/False).
25. The Digital system usually operated on \_\_\_\_\_ system.
26. An Encoder has  $2^n$  input lines and \_\_\_\_\_ output line.
27. BR signal is activated by \_\_\_\_\_.
28. Logic sates can only be \_\_\_\_ or 0.
29. Asynchronous counter are known as \_\_\_\_\_.
30. The Radix of the binary number is \_\_\_\_\_.
31. A floating-point number is said to be normalized if the most significant digit of the mantissa is nonzero. (True/False).
32. The first part represents a signed, fixed-point number called the mantissa. (True/False).
33. The register that holds the address for the stack is called a \_\_\_\_\_.
34. Give full form of RPN.
35. A \_\_\_\_ command is issue to activate the peripheral and to inform it what to do.
36. A \_\_\_\_ command is responsible for transferring data from the bus into peripheral.
37. Address bus is bidirectional. (True/False).
38. Which bus is bidirectional?
39. Stack means \_\_\_\_\_.
40. Floating point representation is used to store \_\_\_\_\_.
41. The circuit used to store one bit of the data is known as \_\_\_\_\_.

## Answer:

1. 1 (one)
2. XOR
3. DEMUX
4. Flip-flop
5. 1 (one)
6. NOT
7. True
8. False
9. Carry and sum
10. Serial in serial out
11. All the input low or '0'
12. Very large scale integration.
13. Eight (8)
14. Veitch diagram.
15. Low or '0'
16. Half adder circuit.
17.  $Y=A'B+AB'$
18. The complement of a sum and The complement of product.
19. True.
20. True.
21.  $(A.B + C.D + E.F)$
22. POS expression.
23. 10
24. True.
25. Binary number system.
26. n bit
27. Clear (CLR) signal.
28. 1 (one)
29. Ripple counter.
30. Two.
31. True.
32. False.
33. Stack pointer.
34. Reverse polish notation.
35. Control command.
36. Output data command.
37. False.
38. Address bus and Data bus.
39. LIFO.
40. Real integers.
41. Flip-flop or latch.