

COA

- 1.What is Flip - Flop ? Explain anyone in detail
- 2.What is Address ? Explain full adder in detail.
- 3.Explain Encoder III detail
- 4.Write a short note on Demultiplexer.
- 5.Explain fixed point representation.
- 6.Explain Parity Bit with Error Detection Code.
- 7.Explain major components of CPU.
- 8.Write a short note on General Register Organization.
- 9.Explain I/O interface III detail.
- 10.Write a short note on rop.

2019

- 1.Explain AND, OR, NOT Logic Gates.
- 2.Explain SR Flip Flop in detail.
- 3.Explain Multiplexer (4 x 1)
- 4.Explain IC in detail.
- 5.Explain error detecting code using parity bit
- 6.Write a note on fixed point representation.
- 7.Explain major components of CPU.
- 8.Explain General Register Organization.
- 9.Explain DMA Controller.
- 10.Explain Input Out Processor (IOP).

2018

- 1.Explain General Register Organization
- 2.Explain ALU
- 3.Explain 4 x 1 Multiplexer
- 4.Write a note on Boolean algebra
- 5.State and prove De - Morgan's theorems.
- 6.Explain stack organization
- 7.Explain DMA Controller
- 8.Explain K-map with example
- 9.Explain Error Detecting Codes.
- 10.Explain Bi-Directional Shift Register

2017

- 1.Explain Karnaugh Map with example.
- 2.What is Flip Flop? Explain SR-flip flop.
- 3.What is decoder? Explain 3 X 8 decoder.
- 4.Explain Asynchronous 4 bit Binary Counter.
- 5.Explain error detecting code using parity bit.
- 6.Write a note on fixed point representation.
- 7.Explain register stack.

- 8.Explain general register organization.
- 9.Write a note on DMA controller.
- 10.Write a note on IOP.

2015

- 1.Explain Stack Organization.
2. Explain Master slave Flip-Flop
- 3.. Explain Polish Notation with its advantages
- 4.Explain general register organization.
- 5.Explain register with parallel load.
- 6.What is combinational circuit? Explain with types.
- 7.What is Flip Flop? Explain with types.
- 8.Prove following Boolean algebra.
 - (a) $AB + A(B+C)+B(B+C)=B+AC$
 - (b) $(X+Y')(X'+Y) =XY + X'Y'$
- 9.Write note on Error Detection Code.
- 10.Explain Asynchronous 4 bit Binary Counter